

VLSI
Exp. No. 6

Redhat Linux

Application → Terminal → csh →
source /home/install/cshrc → virtues →
log window occur

Go to tools → lib manager → file → New
→ library → give name → okay

pop-up below occur → 4 options occur →
select attach to an existing library →
ok

in library part → file → new → cell view →
pop-up come → inside cell → give
name → Type → schematic → ok


new window occur →

shortcut key → 2: open msg add instance
lib → gpdk180
cell → pmos select → ok
— place on screen and then
esc

lib → gpdk180
cell → nmos

wire → press 'w' on keyboard

Sorting body terminal with source

 

select P on keyboard -

Name - Vdd and A

dir → input →

Connect Vdd at source of pmos and nmos

Create one more pin

Name → y

dir → o/p

Click save and check

* if there is an error go to log window and rectify

Changing the width of pmos

select pmos and press 'Q'

change the width $\rightarrow 2\mu\text{m}$ to $4\mu\text{m}$
length $\rightarrow 180\text{nm}$

save check again

Create option \rightarrow Create cell view from cell
view \rightarrow nothing to be changed \rightarrow click ok

symbol generation pin occur

Left pin A

Right pin y

Top pin \rightarrow Vdd

Bottom pin \rightarrow gnd

and then okay

New window will occur

Delete the path name and delete the name
 \rightarrow save check

\rightarrow go back to lib manager

\rightarrow go to file \rightarrow new \rightarrow cell view \rightarrow

pop-up \rightarrow change the name \rightarrow
invert text \rightarrow in invert \rightarrow a

new window will come \rightarrow lib \rightarrow

name inv AAA1 \rightarrow cell \rightarrow inv \rightarrow ok

Outer rectangle should exist which is invisible can be seen when mouse is near to circuit

Press 'I' → lib → analog lib cell → vdc → cell → vdc → hide put on screen

Press 'I' → lib → analog lib cell → v pulse

press 'I' → lib → analog lib cell → gnd

Press 'W' → connect vdc + to vdd.

Press 'P' → name y
dir → output
save check

→ (tool used to simulate circuit)

Launch → Adel → new window

Do some setting → setup → model lib → shows 1 lib 180nm ; if 90 & 45nm is selected, deselect them → okay
→ analysis

go back to test circuit → select vdc → '0'
→ DC voltage : 1.8 (no symbols to be added)

select vpulse → '0' → voltage 1: remain same
voltage 2: 1.8V
period : 20n
(optional)
pulsewidth : 10n

→ ok → save check


→ go to adel → analysis → transient analysis
(voltage on one axis → time on one axis)


→ stop time → 40n → okay


→ window RLS → select setup output

→ new window → from design → it takes
back to test circuit and then click
once on output wire and input wire

→ setting: output → it show → y and net 7

analysis →  tran

 output → , net 7

 R. L. S. → green arrow  → Run

give a waveform window → split all script
→ Right click on input and output and
change colour

Calculation:-

Delay - i.) Rising : 28.5105p
ii.) Falling : 20.974p

$$\text{Propagation delay } (t_p) = \frac{28.5105 + 20.974}{2} = 24.742p$$

Rise time : 56.678p

Fall time : 39.99p